ATUAL				FUTURO					DIAGRAMA DE ESTADOS							
Q0	Q1	Q2	Q3	Q0	Q1	Q2	Q3		JA	KA	JB	КВ	JC	KC	JD	KD
0	0	0	1	0	0	1	1		0	х	0	х	1	х	x	0
0	0	1	1	0	1	0	0		0	х	1	х	х	1	x	1
0	1	0	0	0	1	1	1		0	х	х	0	1	Х	1	х
0	1	1	1	1	0	1	1		1	х	х	1	х	0	х	0
1	0	1	1	1	1	1	0		х	0	1	х	х	0	х	1
1	1	1	0	1	1	1	1		х	0	х	0	х	0	1	х
1	1	1	1	0	0	0	1		х	1	х	1	х	1	х	0
									Q1.Q2	Q1.Q3	Q2	Q3	!Q2	!Q0.!Q1 + Q0.Q1.Q3	Q1	!Q1.Q2
								Sequ	ência util	ncia utilizada						
					Q0=QA				1							
					Q1=QB				3							
					Q2=QC				4							
	J	K	Q		Q3=QD				7							
	0	0	Qn						11							
	0	1	0						14							
	1	0	1						15							
	1	1	!Qn													